

Homework 2 – Logic Gates and Waveforms

Student's Name: _____

Instructions:


- You have to show all work in order to receive full credit

1. A owner of a house wants to design a lamp that works with the following specifications:
 - A lamp in a room is operated from two switches, one at the *front* and one at the *back* of the room.
 - The lamp is to be ON if both of the switches are ON.
 - The lamp is to be OFF if one of the switches is OFF.

According to the description, the best logic gate to perform the operation is (6 pts): _____

2. The number of output combinations for a 6-input logic gate is (6 pts):

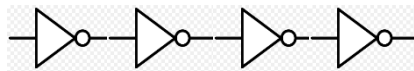3. If four NOT gates are connected in series and the input to the first gate is a **HIGH** (1), the output of the fourth gate will be (6 pts): _____



4. What is the truth table for an **NAND** gate is (6 pts):

Truth Table 2-input NAND gate		
Inputs		Output
A	B	Y
0	0	
0	1	
1	0	
1	1	



5. Given the input A, find the output Y of the given gate (6 pts):





6. Given the input A and B, find the output Y of the given gate (6 pts each):



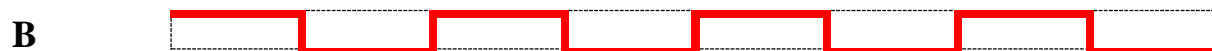
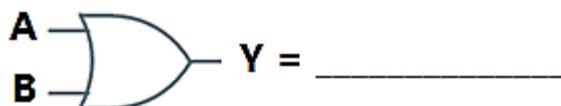
7. Given the input waveform A and B, find the output Y of the given logic gate (11 pts)



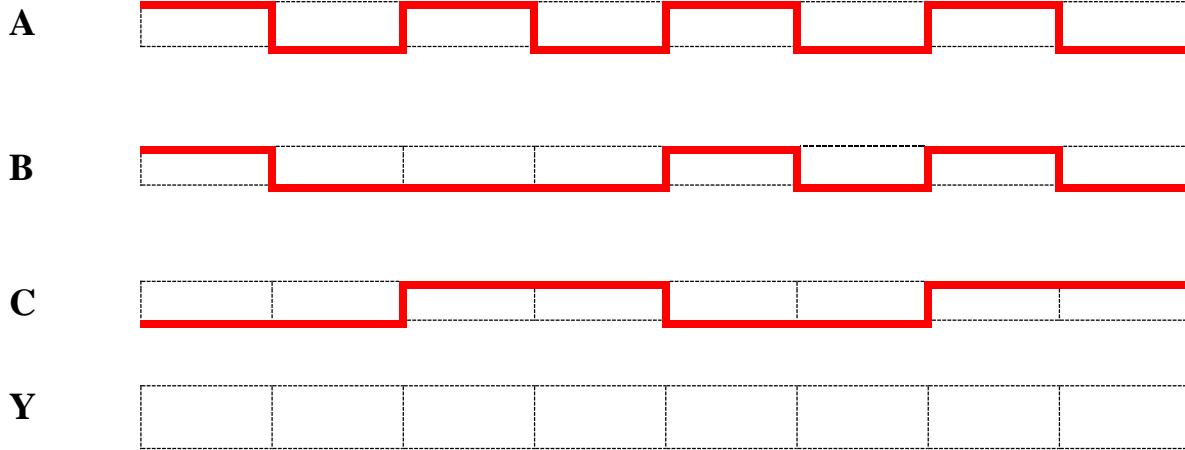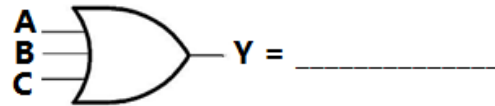1. Given the input waveform A, B, and C, find the output Y of the given logic gate (12 pts)



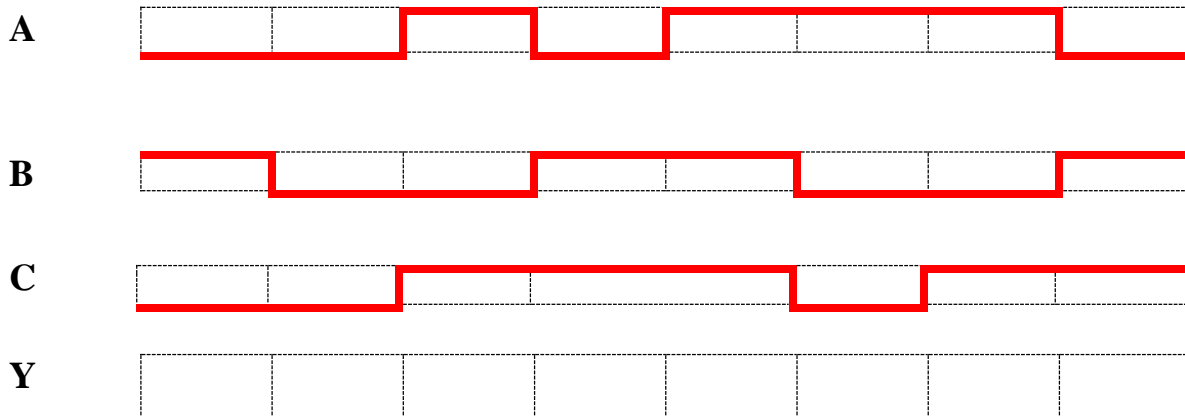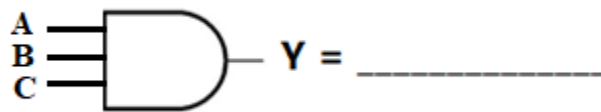2. Given the input waveform A, B, and C, find the output Y of the given logic gate (11 pts)



----- Homework 2 Ends Here -----