

Review - Boolean algebra, DeMorgan's Theorem, Karnaugh Map, and data control circuits

Student's Name _____

Instruction:

- Show all work to receive full credit. Box or circle the answer
-

Question 1

Use Boolean algebra to simplify the following expression $ABC + \overline{A}BC + B\overline{C}$

Sketch the simplified circuit


Question 2

Simplify the following expression using Boolean algebra and DeMorgan's theorem

$$\overline{(\overline{A}B) + \overline{B}C}$$

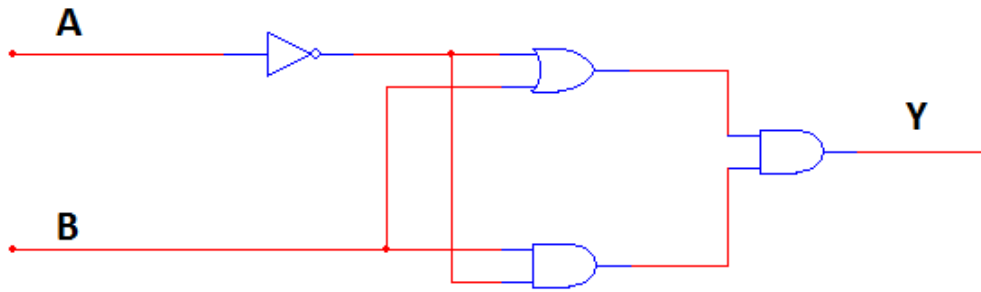Question 3


Find and simplify the output Y of the following logic circuit using Boolean algebra



Draw the simplified circuit

Question 4

Simplify the output X of the following logic circuit using Boolean algebra and DeMorgan's theorem

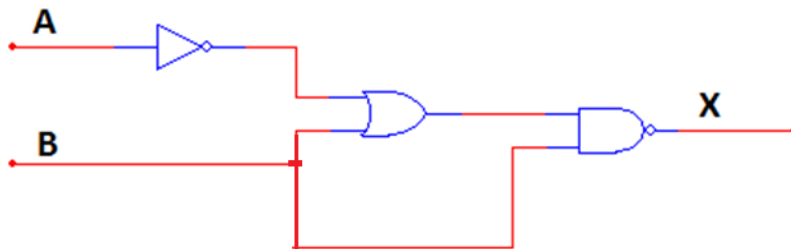

Question 5

Simplify the following Karnaugh Map to its most simplified form:


	$\overline{C}\overline{D}$	$C\overline{D}$	CD	$\overline{C}D$
$\overline{A}\overline{B}$	1	1	0	1
$\overline{A}B$	0	0	1	1
AB	0	0	1	0
$A\overline{B}$	1	1	1	1

Question 6

Simplify the following SOP output $X = \overline{A}\overline{B}C + \overline{A}B\overline{C} + A\overline{B}C + ABC$ using K-map

	\overline{C}	C
$\overline{A}\overline{B}$		
$\overline{A}B$		
AB		
$A\overline{B}$		

Question 7

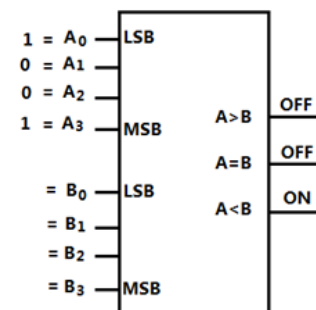


For the following inequality comparator, list all possible inputs for B

Question 8

Design a logic circuit to decode the binary string $A=0010_2$. Assuming that A₀ is the LSB and A₃ is the MSB, write the output equation with respect decoder

Question 9

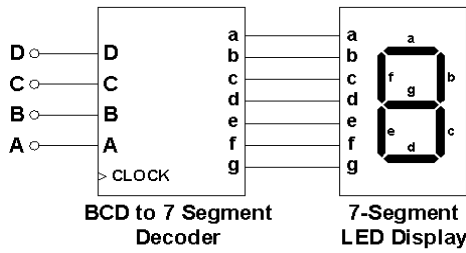


For the following BCD to 7-segment decoder circuit, if we assume that D is the least-Significant-Bit (LSB) and A the Most Significant Bit (MSB)

If we receive the following input, which segment of the 7-segment will be ON? $A = 0, B = 0, C = 1, D = 1$

Segment that will be ON? Write the segment in alphabetic order _____

Question 10

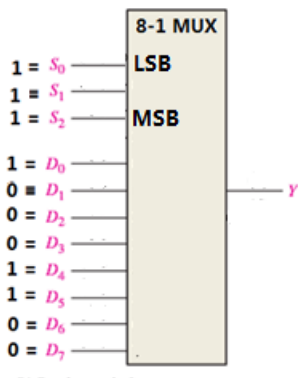


For the following 8-1 MUX, which Data Input is selecting the data selector? _____

What would be output Y? _____

Question 11

Having the following input $A = 1010_2$ and $B = 0011_2$ through the 4-bit full adder below, what would be the output for $\Sigma_3, \Sigma_2, \Sigma_1, \Sigma_0$, and $C_{out(3)}$

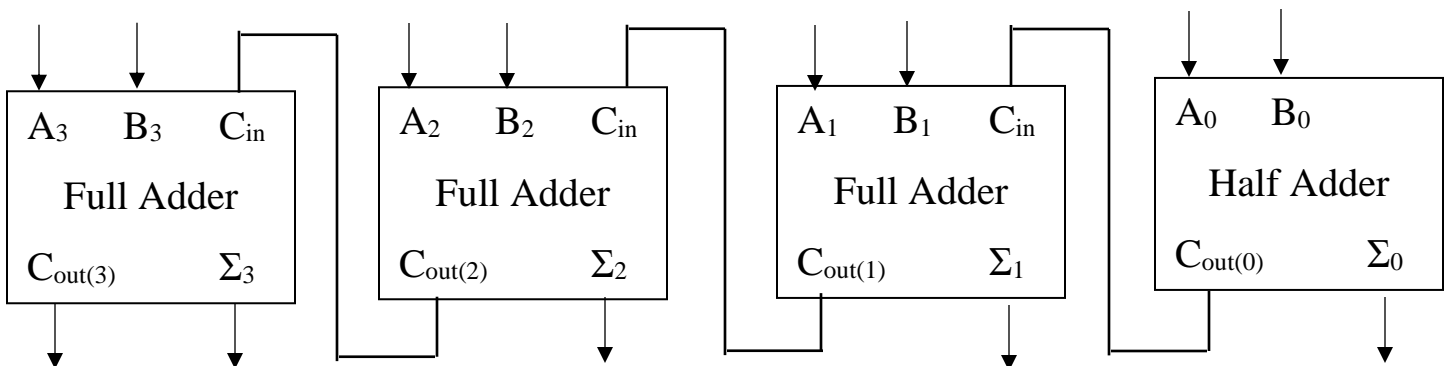


Question 12

For the following 4-bit full-adder circuit, show the bit flow and find SUM_0 , SUM_1 , SUM_2 , SUM_3 , and C_{in} , given:

$A = 0111_2$

$B = 1101_2$

$C_{in} = 0$

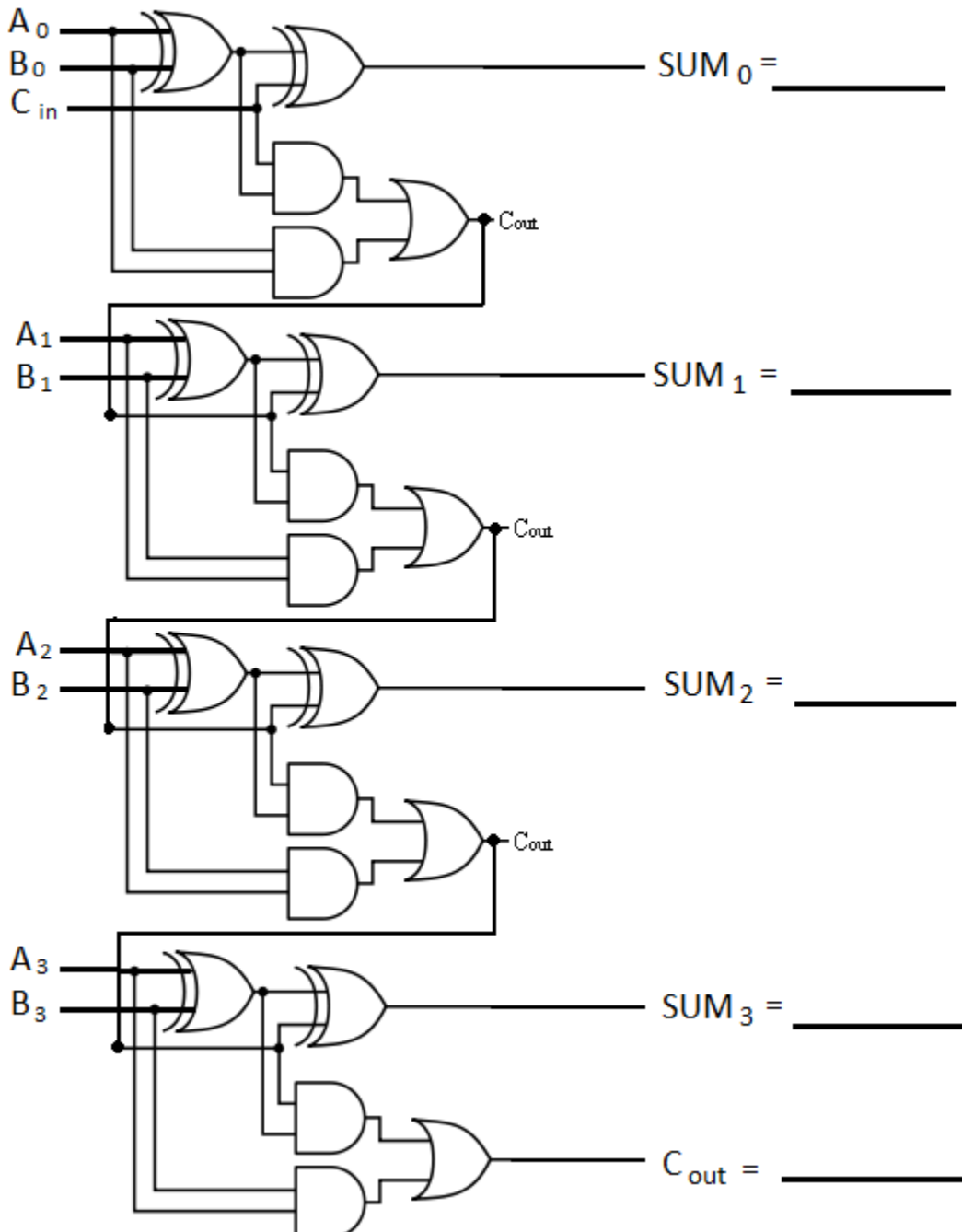

----- Review ends here -----