

Introduction Digital Computing
Homework 2 – Logic Gates and Waveforms

Student's Name: _____

Instructions:

- You have to show all work in order to receive full credit


-
1. The number of output combinations for a 6-input logic gate is: _____
 2. A owner of a house wants to design a lamp that works with the following specifications:
 - A lamp in a room is operated from two switches, one at the *front* and one at the *back* of the room.
 - The lamp is to be ON if both of the switches are ON.
 - The lamp is to be OFF if one of the switches is OFF.

According to the description:

- a) Create a truth table, with all possible inputs combination, that represents the description above

Input		Output
Front switch	Back switch	Lamp

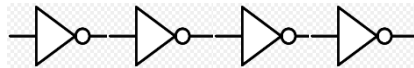- b) According to the truth table in question a), the best logic gate to perform the operation is: _____
3. If four NOT gates are connected in series and the input to the first gate is a **HIGH** (1), the output of the **third** gate is: _____ and the **forth** gate is: _____






4. What is the truth table for an **NAND** gate is:

Truth Table 2-input NAND gate		
Inputs		Output
A	B	Y
0	0	
0	1	
1	0	
1	1	


5. Given the input A, find the output Y of the given gate:



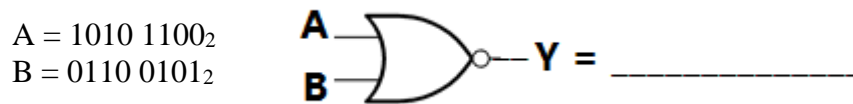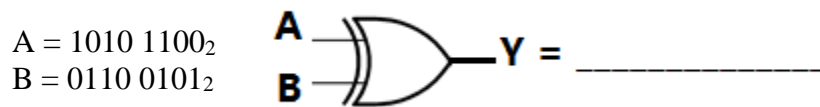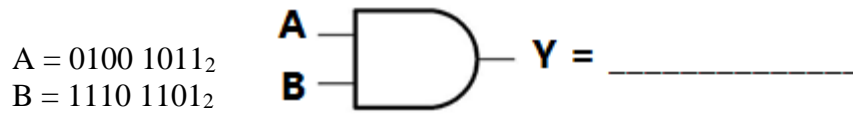6. Given the input A and B, find the output Y of the given gate:



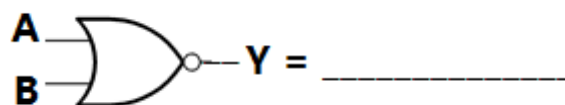7. Given the input waveform A and B, find the output Y of the given logic gate



A




B



Y



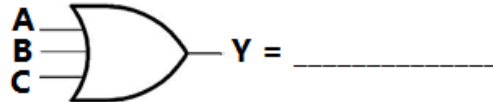8. Given the input waveform A, B, and C, find the output Y of the given logic gate



A




B




C



Y

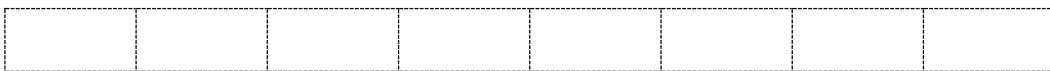

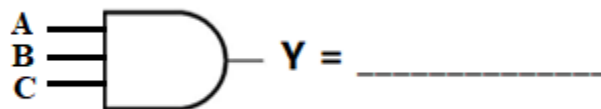
9. Given the input waveform A, B, and C, find the output Y of the given logic gate



A




B

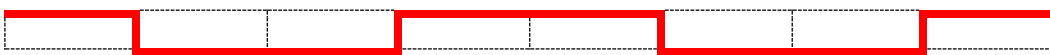

C



Y

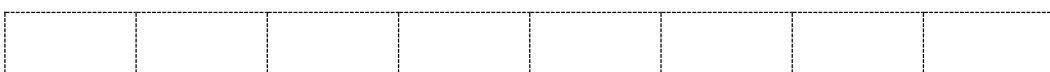

----- Homework 2 Ends Here -----